

## **EXPERIMENT**

### **DOOR BELL USING PUSH BUTTON AND ARDUINO**

#### **CIRCUIT DIGRAM:**

#### **THEORY:**

#### **CONCEPT USED:**

**➤ KIRCHOFF'S VOLTAGE LAW ➤ KIRCHOFF'S CURRENT LAW ➤  
BUZZER BUZZING CONCEPT**

#### **LEARNING & OBSERVATION:**

**• CONNECTIONS IN BREADBOARD AND WIRING • TO FORM  
DIFFERENT PATTERNS FROM LEDS • HOW TO CONTROL ARDUINO &  
ITS CODING • BUZZER CONCEPTS**

#### **OBSERVATIONS:**

**❖ CONTROL OF BUZZER ON PUSH BUTTON ❖ RELATION BETWEEN  
SOFTWARE AND HARDWARE ❖ AUTOMATION OF A DEVICE USING A  
PUSH BUTTON**

#### **PROBLEMS AND TROUBLESHOOTING:**

**✓ TO SELECT THE RIGHT PORT AND TYPE OF ARDUINO ✓ TO CHECK  
THE LOOSE CONNECTIONS ✓ TO CHECK THE CONTINUITY OF CIRCUIT  
✓ TO CHECK THE FLOW OF CURRENT ✓ TO CHECK THE CONNECTIONS  
ACCORDING TO THE CODES ✓ TO CONNECT THE RIGHT PINS IN THEIR  
RESPECTIVE PINMODES ACCORDING TO THE CODES**

#### **PRECAUTIONS:**

**• HANDLE THE COMPONENTS CAREFULLY • AVOID CONNECTING  
ARDUINO TILL THE CIRCUIT IS COMPLETE • CONNECT THE LEDs WITH  
A RESISTANCE TO AVOID DAMAGE • DON'T PLUG THE COMPONENTS  
INTO UNKNOWN CIRCUITS AND MODES**

**SUBMITTED BY: NAME:TUSHAR SRIVASTAVA**

**UID : 19BCS6113**

**COURSE: BE-CSE(AIML-2A)**